

# **CSE 260M / ESE 260**

# **Intro. To Digital Logic & Computer Design**

Bill Siever  
&  
Jim Feher




# This week

- Thursday:  
Studio — Here / Seigle 301
- Midterm Grades: Canvas
  - Studios and Pre-lecture grades posted
  - Hw 1-4 returned / grades posted
  - Exam 1 returned / grades posted



# Exam


# Dff: Setup & Hold Time

 



 
# Dff Time Parameters

- $t_{pcq}$ : Propagation delay from Clock to Q (pcq)
- $t_{ccq}$ : Contamination delay from Clock to Q (ccq)






# Moore Machine: How fast can it go?

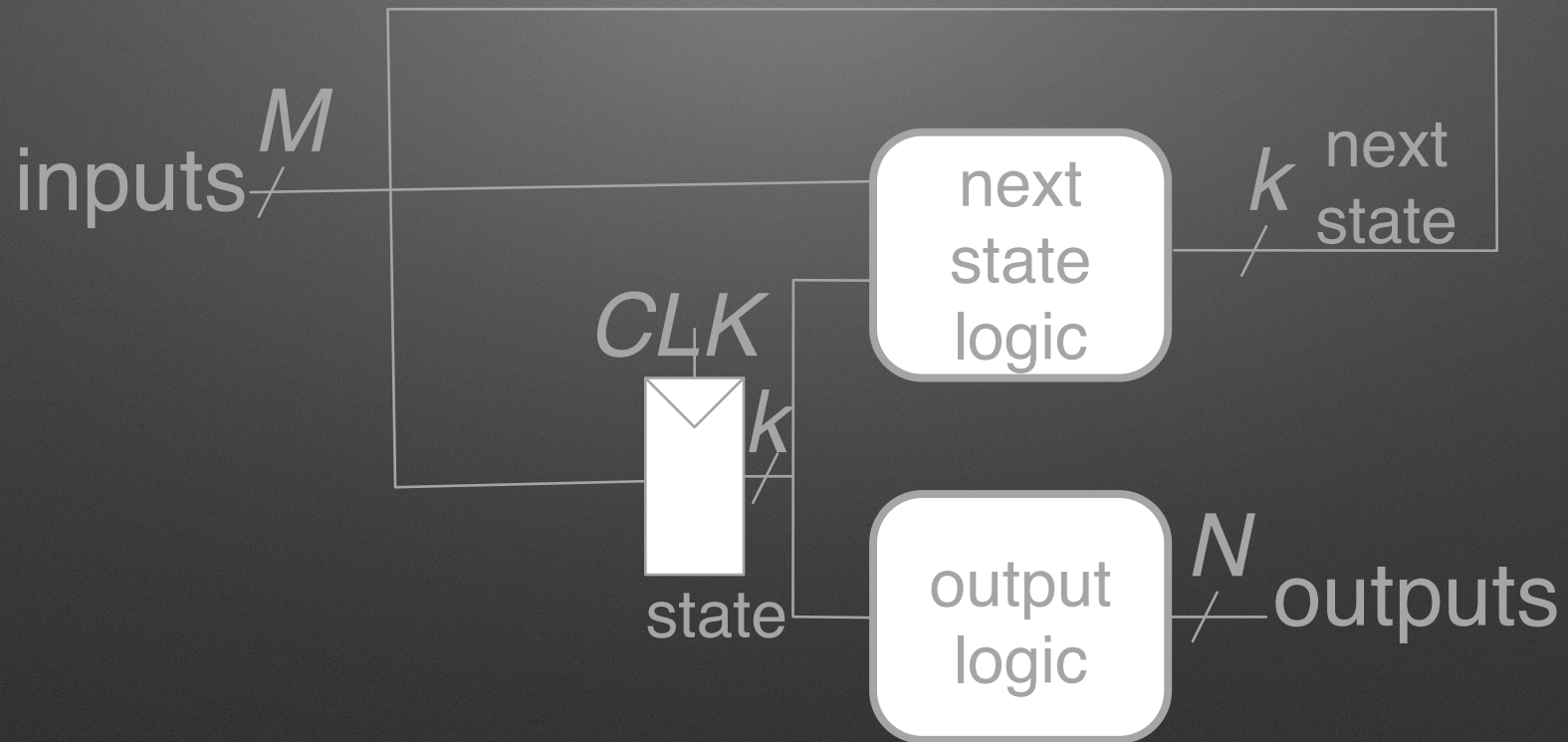



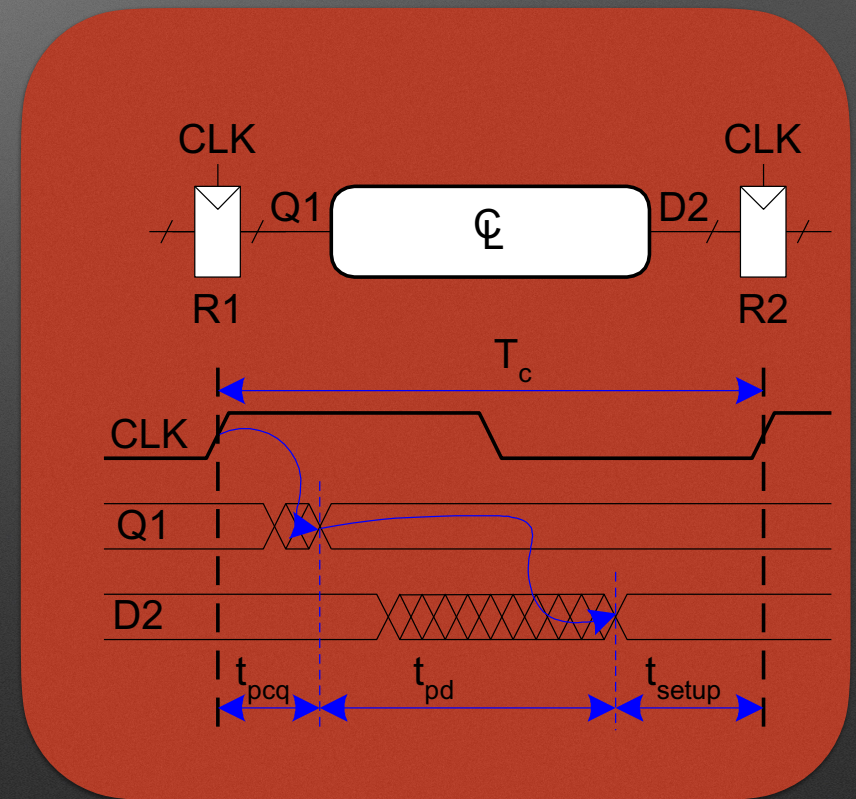
# Fastest Clock Rate?

- R2's input needs to be stable  $t_{setup}$  before clock
- Variation of Moore Machine:  
Imagine no R2 - a loop to R1
- $T_c \geq t_{pcq} + t_{pd} + t_{setup}$


 
# Hold Time Constraint


- Min time from R1 through CL
- R2's input must be stable  $t_{hold}$  after the clock




 
# Hold Time Constraint

- Min time from R1 through CL
- R2's input must be stable  $t_{hold}$  after the clock
- Both  $t_{ccq}$  and  $t_{hold}$  are provided/set
- $t_{cd} \geq t_{hold} - t_{ccq}$   
May need to add delays in Combo. Logic to meet





# Chapter 4



# HDL

- HDL is a way to *describe* hardware
- HDLs typically can describe hardware in different ways
- HDLs describe hardware in modules



# HDLs *Describe* Hardware

- Uses
  - Simulation: Confirm modules work together
  - “Synthesis” : Transformation to real hardware
    - Like compilers used for programming languages
- Description Styles
  - Structure (connect 2 input AND to ...)
  - Behavior (if x then y)



# HDL

- A HDL is not a computer program.
- A HDL is not a computer program!
- A HDL is *not* a computer program!
- A HDL is not a computer program!
- A HDL is **NOT** a computer program!




# We will use Verilog

Not VHDL




# (System) Verilog Module Example

 




# (System) Verilog Module Example

 


```
module example(input logic a, b, c,  
               output logic y);  
    // module body goes here  
endmodule
```

 Input & Output  
are like the Pins  
On chips or in  
JLS





# HDL: Structural (Verilog)

 


```
module nand3(input  logic a, b, c
             output logic y);
    logic n1; // internal signal

    and3 andgate(a, b, c, n1); // instance of and3
    inv  inverter(n1, y);     // instance of inv
endmodule
```



# HDL: Structural (Verilog)

 


```
module nand3(input  logic a, b, c
             output logic y);
    logic n1; // internal signal

    inv inverter(n1, y); // instance of inv
    and3 andgate(a, b, c, n1); // instance of and3
endmodule
```


 
# HDL: Behavioral (Verilog)


```
module nand3(input  logic a, b, c
             output logic y);
    assign y = ~(a & b & c);
endmodule
```




 
# 4-bit mux2: Behavior

- Conditionals via Ternary operator (? :)
- Multi-bit values via [] notation




```
module mux2(input logic [3:0] d0, d1,  
            input logic      s,  
            output logic [3:0] y);  
    assign y = s ? d1 : d0;  
endmodule
```


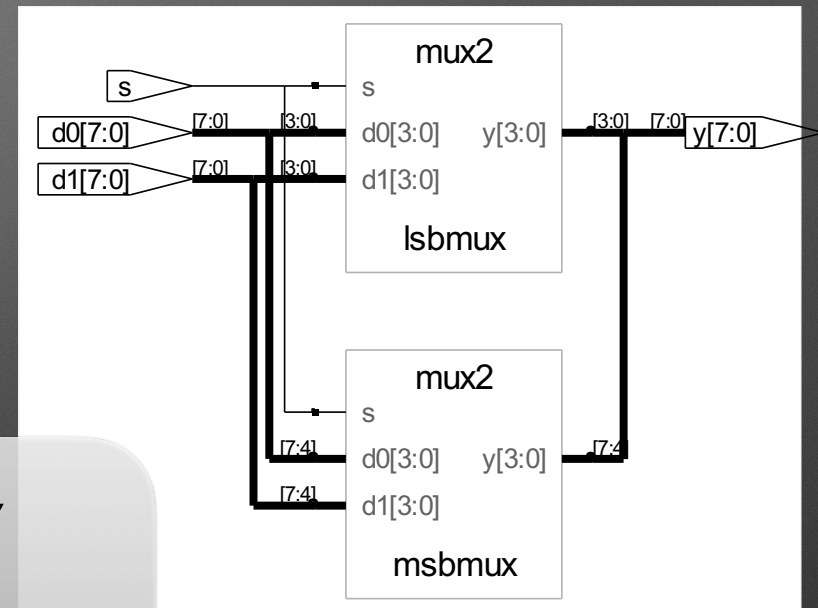
# 8-bit mux2: Hierarchical

```
module mux2_8(input logic [7:0] d0, d1,  
             input logic s,  
             output logic [7:0] y);
```

```
    mux2 lsbmux(d0[3:0], d1[3:0], s, y[3:0]);  
    mux2 msbmux(d0[7:4], d1[7:4], s, y[7:4]);  
endmodule
```





# Sequential Logic



# always: Based on *Events*

- Concept of “event” is related to simulation and “event driven programming”
- JLS uses events: An OR gate “reacts” to events and schedules an update  
See [here](#)




# always Statement

- Form:

```
always @(sensitivity list)
    statement;
```

- When event in sensitivity list occurs, statement is executed


# Verilog: D Flip-Flop

 

```
module flop(input logic clk,  
            input logic [3:0] d,  
            output logic [3:0] q);  
    always_ff @(posedge clk)  
        q <= d; // pronounced "q gets d"  
endmodule
```




# Resettable D-Flip-Flop 1

 

```
module flopr(input logic clk,
             input logic reset,
             input logic [3:0] d,
             output logic [3:0] q);

    always_ff @(posedge clk)
        if (reset) q <= 4'b0;
        else q <= d;
endmodule
```

# Resettable D-Flip-Flop 2

 


```
module flopr(input logic clk,
             input logic reset,
             input logic [3:0] d,
             output logic [3:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else q <= d;
endmodule
```



# Resettable D-Flip-Flop 3

 

```
module flopr(input logic clk,
             input logic reset,
             input logic en,
             input logic [3:0] d,
             output logic [3:0] q);

    always_ff @(posedge clk, posedge reset)
        if (reset) q <= 4'b0;
        else if (en) q <= d;
endmodule
```

# always and Combinational Logic

```
always_comb  
begin  
    y = a & b  
    ...  
end
```

Block of assignments

Could have been done with individual assigns

Notice = ("blocking assignment"), not <= ("non-blocking assignment")



# always\_comb has nice features

- case : Selection between several options  
Great for state machines!
- Must describe all possible combinations to be comb logic. Use default

```
case (state)
  soap:                hot = 1;
  highPressureWarm:    hot = 1;
  ...
  default: hot = 0;
endcase
```

# Questions

- Will we use a HDL? Yes
- [Which HDL?]: Verilog
- Test benches?
- Is my degree worth it? (I think mine was. Your mileage may vary...)



# Next Time

- Studio